

CONTINUOUS INTERNAL EVALUATION - 1

Dept: EC	Sem / Div: ^{A, B, C}	Sub: Basic Electrical Engineering	S Code: 18ELE13
Date: 25/10/19	Time: 3:00-4:30PM	Max Marks: 50	Elective: N


Note: Answer any 2 full questions, choosing one full question from each part.

QN	Questions	Marks	RBT	CO's
PART A				
1	<p>a Define KVL and obtain the potential difference between X-Y and M-N in the fig 1(a)</p>	10	L3	CO1
	<p>b A capacitor of 50μF shunted across a non inductive resistor of 100Ω is connected in series with a resistor of 50Ω and the circuit is connected to 200V, 50Hz supply. Find the i) circuit current ii) voltage across 100Ω and 50Ω resistor and power factor.</p>	8	L3	CO1
	<p>c Derive the RMS and average value of sinusoidal voltage in terms of its maximum value.</p>	7	L2	CO1
OR				
2	<p>a Find the value of R shown in fig 2(a) so that the current drawn from the circuit is 250mA. Also find the current i1 and i2</p>	8	L3	CO1
	<p>b A voltage of $v=100\sin 314t$ is applied to a circuit consisting of 25Ω resistor and 80μF capacitor in series. Determine i) peak value of current ii) power factor iii) total power consumed by the circuit</p>	7	L3	CO1
	<p>c With the aid of phasor diagram obtain the relationship between the line and phase values of star connected system. Also derive the expression for power in a star connected system.</p>	10	L2	CO1
PART B				
3	<p>a A voltage of 200V, 50Hz is applied to a series circuit consisting of a resistor, an inductor and a capacitor. The respective voltage across these components are 170V, 150V and 100V. The current drawn by the circuit is 4A. Find the value of R, L and C of the circuit. Also calculate the power</p>	10	L3	CO1

Sowmya Anil

Prepared by: Mrs Sowmya Anil

S. Kant
HOD

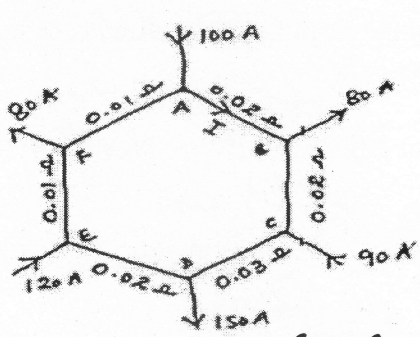	factor of the circuit.			
b	A circuit consist of 2 parallel resistor having resistance 20Ω and 30Ω respectively connected in series with 15Ω resistor. If current through 30Ω resistor is $1.2A$ i) find the current through 20Ω and 15Ω resistor ii) The voltage across 15Ω and 20Ω resistors and iii) total power in the circuit.	8	L3	CO1
c	State the advantage of three phase over single phase.	7	L2	CO1
OR				
4 a	State ohms law and mention its limitations.	6	L2	CO1
b	Find the current in various branches in the circuit shown in <i>fig 4(b)</i>	6	L3	CO1
 <p style="text-align: center;"><i>fig 4(b)</i></p>				
c	A balanced star connected load of $(8+j6)\Omega$ per phase is connected to a three phase $230V$ supply. Find the line current, power factor, reactive power and total power in the circuit.	6	L3	CO1
d	With neat sketch briefly explain how an alternating voltage is produced when a coil is rotated in a magnetic filed.	7	L3	CO1